

## Solution:

$$E_A = 1 \angle 0^\circ \\ = 1 + j0.0 \text{ pu}$$

for a line to ground fault the fault impedance is

$$j0.25 + j0.35 + j0.1 = j0.7$$


the positive sequence impedance may be less than the negative sequence impedance.

$$I_A^{(1)} = \frac{E_A}{z^{(1)} + z^{(2)} + z^{(0)}} = \frac{1 + j0.0}{j0.7} = -j1.428$$

for LG fault:  $I_A^{(1)} = I_A^{(2)} = I_A^{(0)} = -j1.428$

the pu fault current:
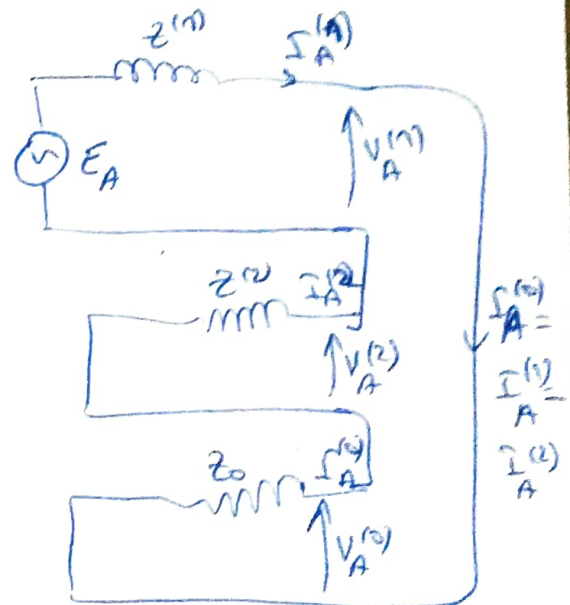
$$I_A = I_A^{(1)} + I_A^{(2)} + I_A^{(0)} = 3I_A^{(1)} = -j4.285$$



interconnection of sequence Network.

Let the base quantities be 25 MVA, 13.2 kV and hence

$$\text{the base current} = \frac{25 \cdot 1000}{\sqrt{3} \cdot 13.2} = 1093 \text{ Amps}$$

The fault current in amperes =  $1093 \times 4.285 = 4685$  Amps

to find out the voltages, we first find out the sequence components of voltages.

$$V_A^{(1)} = E - I_A^{(1)} Z^{(1)}$$

$$= 1 + j0.0 - (-j1.428)(j0.25) = 1 - 0.357 = 0.643$$

$$V_A^{(2)} = -I_A^{(2)} Z^{(2)} = -(-j1.428)(j0.35) = -0.4998$$

$$V_A^{(0)} = -I_A^{(0)} Z^{(0)} = -(-j1.428)(j0.1) = -0.1428$$

As a numeric check  $V_A = 0$ . Substituting the values of  $V_A^{(1)}, V_A^{(2)}, V_A^{(0)}$   
 $0.643 - 0.4998 + 0.1428 = 0$

$$V_B = V_B^{(1)} + V_B^{(2)} + V_B^{(0)} \text{ and } V_C = V_C^{(1)} + V_C^{(2)} + V_C^{(0)}$$

$$* V_B^{(1)} = a^2 V_A^{(1)} = (-0.5 - j0.866)(0.643) = -0.3215 - j0.5568$$

$$V_B^{(2)} = a V_A^{(2)} = (-0.5 + j0.866)(-0.50) = 0.25 - j0.433$$

$$V_B^{(0)} = V_A^{(0)} = V_B^{(0)} = -0.1428$$

$$* V_C^{(1)} = a V_A^{(1)} = (-0.5 + j0.866)(0.643) = -0.3215 + j0.5568$$

$$V_C^{(2)} = a^2 V_A^{(2)} = (-0.5 - j0.866)(-0.5) = 0.25 + j0.433$$

$$\rightarrow V_B = -0.3215 - j0.5568 + 0.25 - j0.433 - 0.1428 = -0.2143 - j0.9898$$

$$\rightarrow V_C = -0.3215 + j0.5568 + 0.25 + j0.433 - 0.1428 = -0.2143 + j0.9898$$

Now, the Line-to-Line Voltage

$$V_{AB} = V_A - V_B \text{ - Since } V_A = 0$$

$$V_{AB} = -V_B = 0,2143 + j0,9898$$

$$V_{AC} = -V_C = 0,2143 - j0,9898$$

$$V_{BC} = V_B - V_C = -j2 \times 0,9898 = -j1,9796$$

Now

$$V_{AB} = 0,2143 + j0,9898 = \sqrt{(0,4592 + 9,797) \times 10^{-1}} = \sqrt{10,2562} = 3,2025$$
$$= \sqrt{1,0346} = 1,0127 \text{ p.u.}$$

The Line-to-Line voltage will be

$$V_{AB} = 1,0127 \cdot \frac{13,2}{\sqrt{3}} = \boxed{7,717 \text{ kV}}$$

$$V_{AC} = \boxed{7,717 \text{ kV}}$$

$$V_{BC} = 1,9796 \times \frac{13,2}{\sqrt{3}} = \boxed{15,08 \text{ kV}}$$

## Solution: Ex 2

Two generators operate in Parallel,

$$x_1 = j \frac{0.09}{2} = j 0.045 \text{ pu}$$

$$x_2 = j \frac{0.05}{2} = j 0.025 \text{ pu}$$

$$Z_0 = j 0.04 + 3 R_n = \left( j 0.04 + 3 \times \frac{1 \times 12}{(11)^2} \right) \text{ pu}$$
$$= (0.297 + j 0.04) \text{ pu}$$

a/ fault currents

$$I_f = I_a = 3 I_a^{(1)} = \frac{3 E_a}{X^{(1)} X^{(2)} + Z^{(0)}}$$

$$I_f = \frac{3 \cdot 1.0}{(j 0.045 + j 0.025 + 0.297 + j 0.04)}$$
$$= \frac{3}{(0.297 + j 0.11)} = \frac{3}{0.3167 \angle 20.32^\circ} = 9.472 \angle -20.32^\circ \text{ pu}$$

b/ Current in the grounding resistor

$$I_f = 9.472 \times \frac{12}{\sqrt{3} \times 11} \text{ kA} = 5.96 \text{ kA}$$

c/ Voltage across grounding resistor

$$= \frac{1 \times 12}{11^2} \times 9.472 = 0.939 \text{ pu}$$

$$= 0.939 \times \frac{11}{\sqrt{3}} = 5.96 \text{ kV}$$